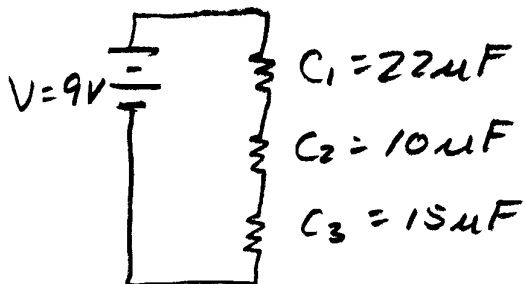


Capacitor Quiz - 05-12-04 *Ch. 16*

$$1/C_{eq} = 1/C_1 + 1/C_2 + 1/C_3 \quad C_{eq} = C_1 + C_2 + C_3 \quad Q = CV \quad C = k\epsilon_0 A/d \quad \epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$

1. Three capacitors ($C_1 = 22 \mu\text{F}$, $C_2 = 10 \mu\text{F}$, and $C_3 = 15 \mu\text{F}$) are in series with a 9 V battery. Draw diagram.
 (a) What is the equivalent capacitance? (b) What is the charge on C_1 ? (c) What is the voltage across C_1 ?



$$Q_{eq} = C_{eq} V$$

$$= 4.71 \mu\text{F} (9 \text{ V})$$

$$Q_{eq} = 42.4 \mu\text{C}$$

b) $Q_1 = 42.4 \mu\text{C}$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$= \frac{1}{22 \mu\text{F}} + \frac{1}{10 \mu\text{F}} + \frac{1}{15 \mu\text{F}}$$

$$Q_1 = C_1 V_1$$

$$V_1 = \frac{Q_1}{C_1}$$

$$= \frac{42.4 \mu\text{C}}{22 \mu\text{F}}$$

a) $C_{eq} = 4.71 \mu\text{F}$

c) $V_1 = 1.93 \text{ V}$

2. You need to design a parallel plate capacitor to have $C = 22 \times 10^{-9} \text{ F}$. If you use polystyrene, which has a dielectric constant of 2.56, and the spacing is half a millimeter, what area of plate should you use?

$$C = \frac{k\epsilon_0 A}{d}$$

$$A = \frac{Cd}{k\epsilon_0}$$

$$= \frac{22 \times 10^{-9} \text{ F} (0.0005 \text{ m})}{2.56 (8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2})}$$

$A = 0.486 \text{ m}^2$